

S20220010039
Sec-9

Digital Logic Design
Mid-2 Semester Exam

Indian Institute of Information Technology Sri City, Chittoor

Date: 23/01/2023

Time 90 Mins

Maximum Marks 25M

Instructions

- A. All questions are compulsory
- B. Each question carries equal marks (5M).
- C. If required, consider the necessary assumptions.

1. Simplify the Boolean function $F1 = P + Q$ using K-map and draw the circuits using NAND gates where $P = \sum(1, 4, 6, 7, 9, 10, 13, 14)$,

$$Q = \sum(2, 3, 8, 9, 13, 14, 15)$$

[5 M]

2. Write the truth table of full subtractor and implement using Multiplexers.


[5 M]

3. Write truth table and the Boolean expressions for equal, greater and lesser of a 1-bit magnitude comparator and draw the circuit.

[5 M]

4. Write the Boolean expressions for all internal wires (carry, DO, D1, D2, D3) and outputs (Sum and Y).

[5 M]

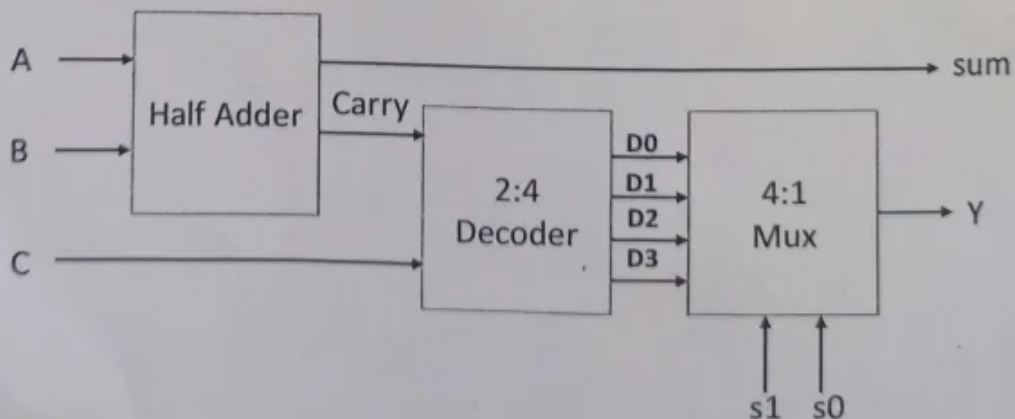

5. Design 4-bit BCD adder assuming a 4-bit binary adder is available.

[5 M]