

DLD, End Term Exam
Indian Institute of Information Technology, Sri city, Chittoor, AP
(An Institute of National Importance)

Date: 8-Dec-2023

Time: 90 Mins

Maximum Marks: 25 M


Instructions:

- A. All questions are compulsory. There is a internal choice for question 5.
- B. Each question carries equal marks (5M).
- C. Electronic gadgets including calculators are not allowed in the examination.
- D. If required, consider the necessary assumptions.
- E. It is compulsory to write the roll number and section number on the question paper.
- F. Attach the question paper to the answer script.

Roll Number..... S202310153 S 2023 00 1015 3 Section: 2

✓ 1. Design an Asynchronous down counter that counts from 15 to 0 and then repeats itself.

 ✓ 2. Determine the state equation, state table, and draw the state diagram for the following sequential circuit. Assume that A and Z indicate the input and output, respectively.




✓ 3. Design a mod-5 synchronous counter using T-flip flop.



(P.T.O)

4. a. Draw the state diagram of J-K flipflop and convert D Flipflop to J-K Flipflop (3M)

 
4.b. Draw the output waveform of a D-latch enable at positive level and positive edge triggered D-flipflop. The input and clock signal is shown below. (2M)



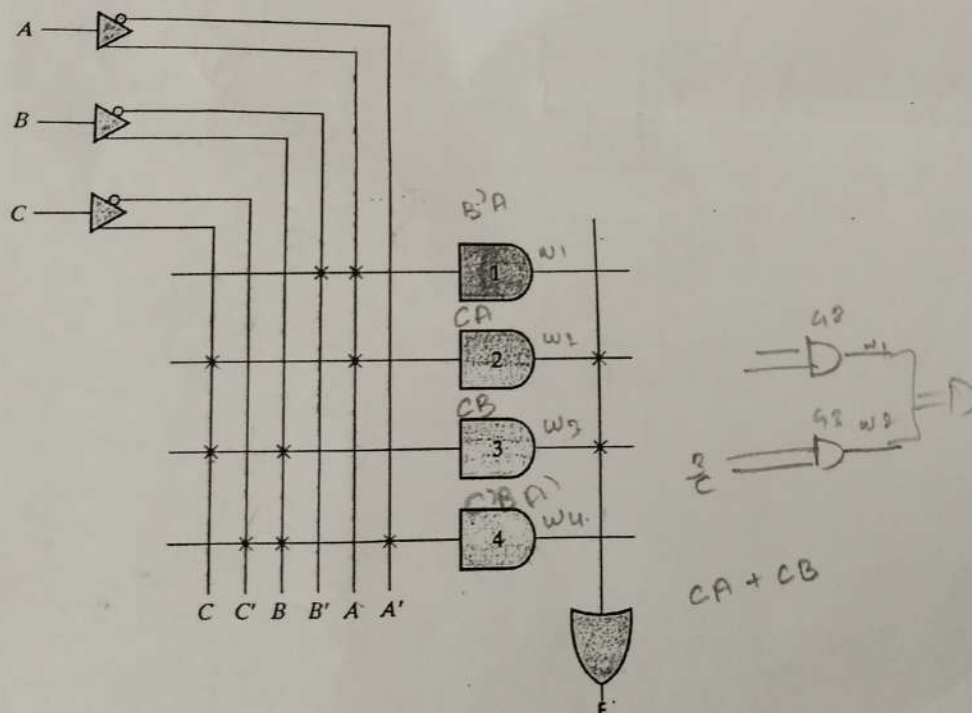5. Draw the circuit diagram of a 4-bit PISO register using D-FFs and explain the operation. (5M)

(or)

Write a Verilog HDL program to implement the following digital circuit where A, B and C are inputs and F denotes the output. (5M)



(End of the paper)