



MID EXAMINATION –Spring 2026

Basic Electronics Circuits

UG1 (PC)

Duration: 90 Mins(2:30 to 4 PM)

Date: 24-02-2026



Max. Marks: 25


Instructions:

Roll I



1. Closed book exam
2. Calculators are allowed. Sharing in exam hall is strictly not allowed
3. Assumptions made should be clearly stated
4. All sub-parts of the question should be written together
5. Question paper must be attached with the answer booklet

Section-A

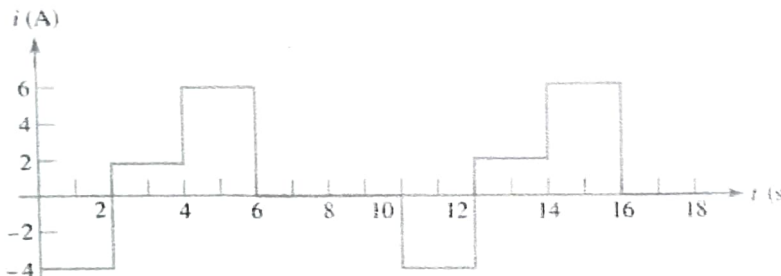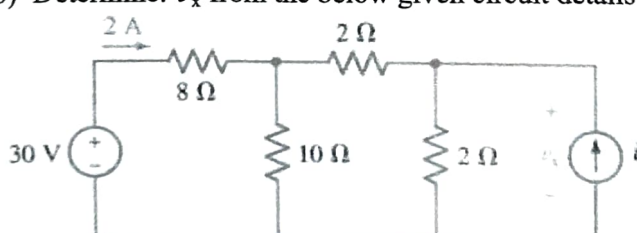1	a) Figure Shown below has a period of 10 seconds. i) What is the average value of the current over one period ii) How much charge is transferred in the interval $1 < t < 12$? 	2 M
	b) Determine: v_x from the below given circuit details 	2 M
	c) Define Voltage	1M
2	a) Derive L_{eq} for a parallel combination of Inductors	1.5 M
	b) Use Ohm's law and Kirchoff's laws on the circuit below and find i) v_x ii) i_{in} iii) Power provided by the dependent source and justify	3.5 M

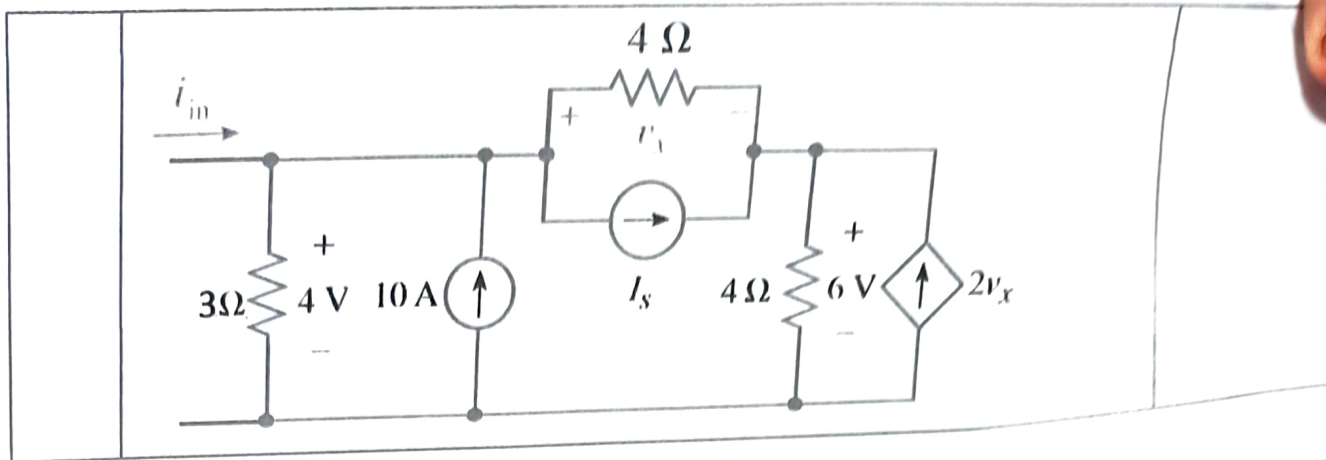

Section-B

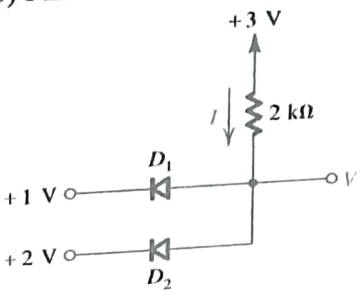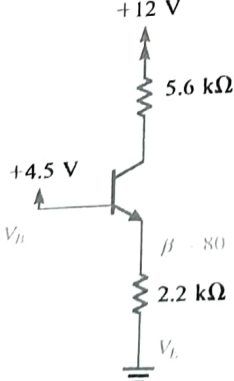3	a) Explain PN junction with a neat diagram indicating Majority, Minority and bound charges, Depletion region indicating the Diffusion and Drift currents for forward bias of the Diode	2 M
	b) Find V and I from the below circuit assuming Diodes are ideal 	1 M
	c) Explain BJT in Common Emitter configuration and Active mode with a Diagram Explaining the minority and majority charge distributions at Emitter-Base Junction and Collector-Base Junction	2 M
4	a) Comment on the mode of the circuit given below to determine the voltages at all nodes and the currents through all branches, Assume that β is specified to be 80 $V_{CC}=+12\text{ V}$, $V_B=+4.5\text{ V}$, $R_C=5.6\text{ k}\Omega$, $R_E=2.2\text{ k}\Omega$, $V_{BE}=0.7\text{ V}$ 	3M

	b) Explain briefly NPN amplifier and Voltage-Transfer Characteristics and derive $i_c = g_m v_{be} \quad \text{where} \quad g_m = \frac{I_c}{V_T}$	2M
5	a) Derive the expression of Ripple voltage for a shunt capacitor filter b) Using a Diode bridge circuit with RC filter and a Zener diode will be in parallel with the output load. An ac input voltage with RMS value 230 V and at 60 Hz is available. Zener diode with $V_{zo} = 15 \text{ V}$ ($I_z = 50 \text{ mA}$) and resistance of 3 ohms. And a transformer with an 10:1 turns ratio is available. Diode cut-in voltage = 0.8 V, Ripple voltage = 1.5 V, $R_L = 600 \text{ ohms}$, and $R = 250 \text{ ohms}$. Determine, V_s (peak), V_{o1} (voltage across the capacitor), V_o.	2M 3 M

***** All the Best *****